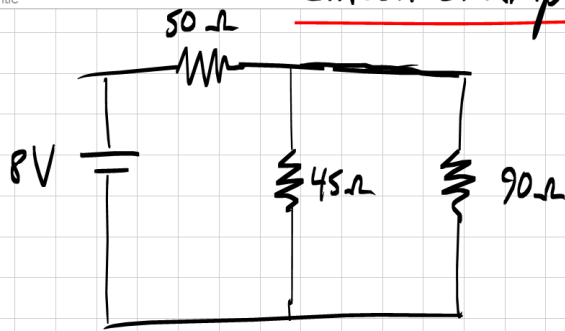



Essential Circuit Example Solutions

CIRCUIT EXAMPLES



$$\frac{1}{R_{eq}} = \frac{1}{45} + \frac{1}{90}$$
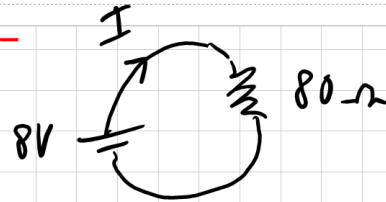
$$\frac{1}{R_{eq}} = \frac{3}{90} \Rightarrow R_{eq} = 30 \Omega$$



$$R_T = 30 \Omega + 50 \Omega$$

$$R_T = 80 \Omega$$

①

$$V_T = I_T R_T$$

$$8V = I_T (80 \Omega)$$

$$I_T = 0.1A$$

②

VOLTAGE DROP ACROSS 50 Ω RESISTOR

$$V_1 = I_1 R_1 \\ = (0.1A)(50)$$

$$V_1 = 5V$$

③

VOLTAGE DROP ACROSS 45 Ω OR 90 Ω

$$8V = 5V + ?$$

$$3V \text{ Drop Across } 45 \Omega$$

④


CURRENT THROUGH 45 Ω RESISTOR

$$V = IR$$

$$3V = I 45 \Omega$$

$$I = 0.066 \text{ Amps}$$

$$3V \text{ Drop Across } 90 \Omega$$

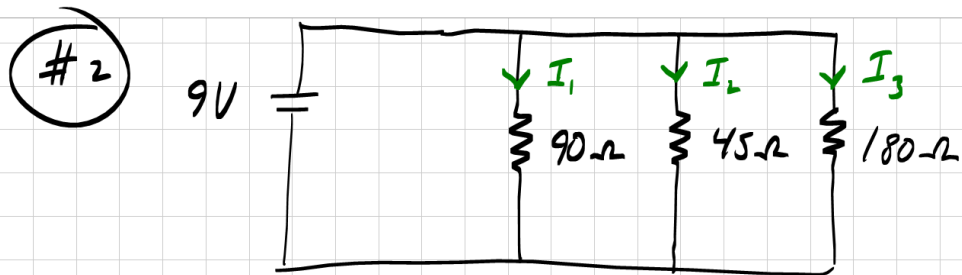

a) NOTE VOLTAGE DROP ACROSS EACH RESISTOR IS 9V!

$$V = IR$$

$$I_1 = \frac{V}{R} = \frac{9}{90} = \underline{0.1 \text{ Amps}}, \quad I_2 = \frac{V}{R} = \frac{9V}{45\Omega} = \underline{0.2 \text{ A}}$$

$$I_3 = \frac{V}{R} = \frac{9}{180V} = \underline{0.05 \text{ A}} \quad I_T = I_1 + I_2 + I_3$$

$$I_T = 0.1 + 0.2 + 0.05$$

$$I_T = \underline{0.35 \text{ A}}$$

b) $\frac{1}{R_T} = \frac{1}{90} + \frac{1}{45} + \frac{1}{180}$

$$\frac{1}{R_T} = 0.011 + 0.0222 + 0.00555$$

$$R_T = \underline{26 \Omega}$$

#3

FIND R

$$V_T = I_T R_T$$

$$10V = 2A (R_T)$$

$$R_T = 5\Omega$$

(TOTAL RESISTANCE)

OF CIRCUIT

$$R = 5\Omega - 2\Omega$$

$$R = 3\Omega$$


FIND POWER GIVEN OFF BY R:

$$P = I^2 R$$

$$P = (2)^2 (3\Omega)$$

$$P = 12 \text{ WATTS}$$

#4

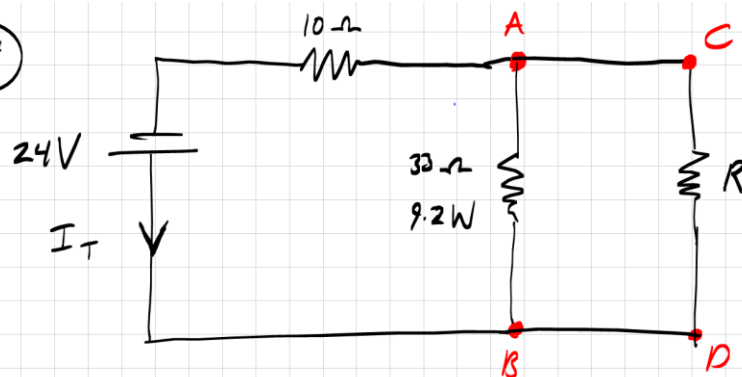

① V_{AB}

$$P = \frac{V^2}{R}$$

$$9.2W = \frac{V^2}{33}$$


$V_{AB} = 17.4V$ ✓

FIND ANY
VALUES
YOU CAN
SOLVE
FOR THEN...
SOLVE FOR
MORE

② $V_{10\Omega} \rightarrow 24V - 17.4V = 6.6V$ ✓

ALSO $\rightarrow V_{CD} \rightarrow V_{CD} = V_{AB}$ { PARALLEL } $V_{CD} = 17.4V$ ✓

③

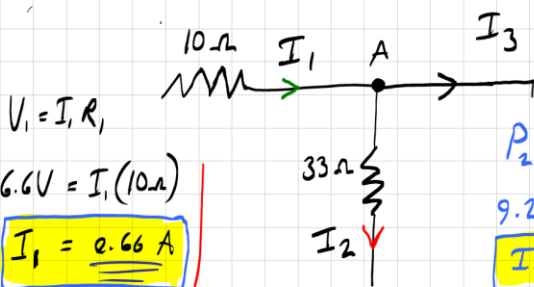

$V_1 = I_1 R_1$

$6.6V = I_1 (10\Omega)$

$I_1 = 0.66A$

$P_2 = I_2^2 R_2$

$9.2W = I_2^2 (33)$

$I_2 = 0.528$

$I_1 = I_2 + I_3$

$0.66A = 0.528 + I_3$

$I_3 = 0.132A$

$P_T = P_1 + P_2 + P_3$ (ADD UP ALL POWER DISSIPATION)

$P_T = \frac{(6.6V)^2}{(10\Omega)} + (9.2W) + (0.132A)(17.4V)$

$P_T = 4.356 + 9.2 + 2.29$

$P_T = 15.85W$ ← TOTAL POWER USED UP BY CIRCUIT.

#5

$$V_T = I_T R_T$$

$$80V = I_T R_T$$

$$80V = I_T (26.8\Omega)$$

$$I_T = 2.985A$$

TOTAL

$$R_T = 12 + 10 + R_{eq}$$

$$R_T = 12 + 10 + 4.8$$

$$R_T = 26.8\Omega$$

$$\frac{1}{R_{eq}} = \frac{1}{12} + \frac{1}{8}$$

$$R_{eq} = 4.8\Omega$$

12Ω RESISTOR	$V_1 = I_T (R_1)$ $V_1 = (2.985A)(12\Omega)$ $V_1 = 35.8V$	$V_2 = I_2 R_2$ $V_2 = (2.985A)(10\Omega)$ $V_2 = 29.85V$	10Ω RESISTOR
------------------------	--	---	---------------------

$$P = \frac{V^2}{R}$$

$$P = \frac{(14.35V)^2}{8\Omega}$$

$$\begin{aligned} V_3 & 80V = V_1 + V_2 + V_3 \\ 80V & = 35.8V + 29.85V + V_3 \\ V_3 & = 14.35V \end{aligned}$$

(VOLTAGE OVER 8Ω AND 12Ω RESISTORS)
IN PARALLEL

$$P = 25.74W$$

POWER DISSIPATED BY
 8Ω RESISTOR. 😊