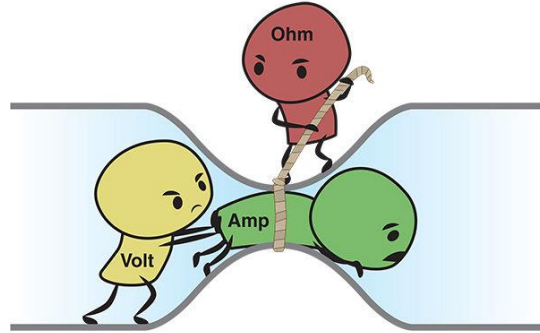


# Ohm's Law



The most important relationship for helping to understand circuits

$$I = \frac{V}{R}$$



Look at the equation above. Ohm's law is an equation that simply represents the following:

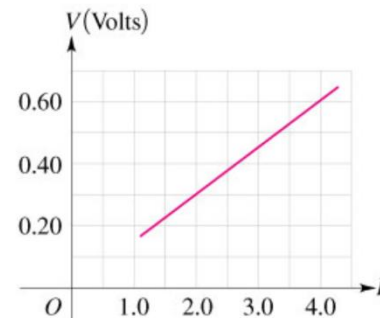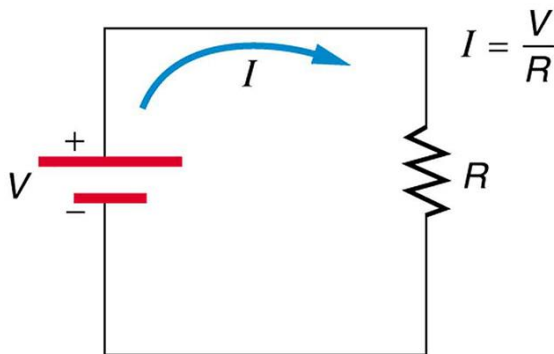1. **MORE Voltage** (Energy) means **MORE current flow** you will get.
2. **MORE Resistance** means **LESS current flow**.



Ohm's Law is more commonly written as:

$$V = IR$$

$$V = IR$$


**Examples:**

Below is a very simple circuit with a battery and a resistor. The battery is a 12 volt battery, and the resistance of the resistor is 600 Ohm. How much current flows through the circuit?

$$I = V/R$$

$$I = 12 \text{ V}/600 \text{ Ohm}$$

$$I = 0.02 \text{ A}$$

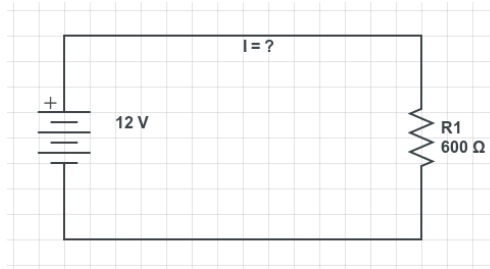

So the current in the circuit is 0.02 Amps or 20 mA.


**Note:** 1 Amp = 1000 milliamps (1 A = 1000mA)

Below we have a circuit with a resistor and a battery again. But this time we don't know the voltage of the battery. What Voltage must the battery be supplying?

$$V = IR$$










$$V = (0.03 \text{ Amps}) \times (600 \text{ Ohms})$$

$$V = 1.8 \text{ V}$$

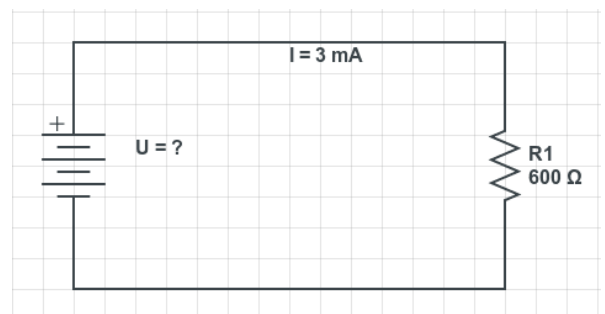

So the voltage of the battery must be 1.8 V.

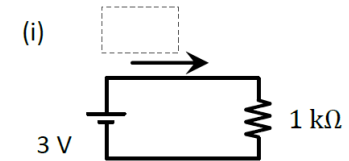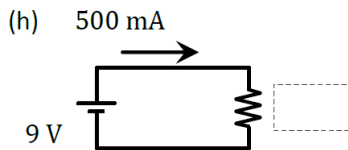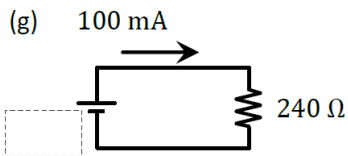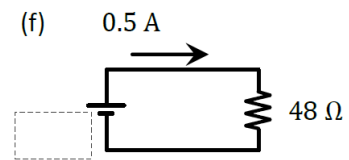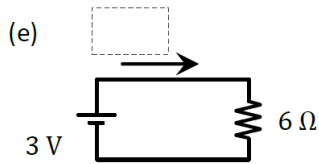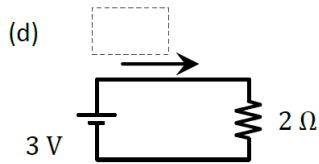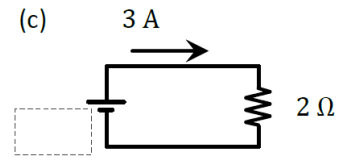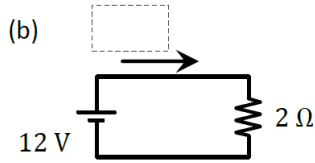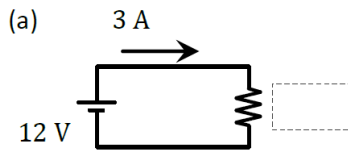1. Use ohm's Law to determine the missing values in the circuits below. **Watch your units.**



Answers

- a)  $4 \Omega$
- b)  $6 \text{ A}$
- c)  $6 \text{ V}$
- d)  $1.5 \text{ A}$
- e)  $0.5 \text{ A}$
- f)  $24 \text{ V}$
- g)  $24 \text{ V}$
- h)  $18 \Omega$
- i)  $0.003$